

Exercises with Finite State Machines

CS 64: Computer Organization and Design Logic
Lecture #17

Ziad Matni
Dept. of Computer Science, UCSB

FINAL IS COMING!

- **Wednesday, 6/13** in this classroom
- **Starts at 12:00 PM **SHARP****
 - Please start arriving 10-15 minutes before class
- **I may ask you to change seats**
- Please bring your UCSB IDs with you
- **Closed book: no calculators, no phones, no computers**
- **Only the MIPS Reference Card is allowed**
- **You will write your answers on the exam sheet itself.**



What's On the Final Exam?

- Everything

What's On the Final Exam?

- Binary Arithmetic
- MIPS Assembly Language
 - Programming
 - Instructions
 - MIPS Calling Convention
- Digital Logic Design
 - Simplification using Logic Arithmetic, TTs, & Kmaps
 - Combinatorial design, incl. muxes, ALUs
 - Sequential design, incl. latches, DFF
 - Finite State Machine design

To Review

- ALL the class lectures and demos
- Your notes
- MIPS Reference Card
- ALL the class labs
 - If you get any Ethics/Impact of CS questions, they'd be short/M.C. questions...

Lecture Outline


- FSM Exercises

Any Questions From Last Lecture?

FSM Exercise 1

- Given a FSM described with the following state diagram where:

 
- The initial state is S1
- There is only 1 input, X
- There is only 1 output, Y, and it is initialized to 0



- What state do you end up in if X takes on the sequential values 0110?
- Which of these inputs will result in $Y = 1$ at the end of their sequences?
 - A. 0110
 - B. 1111101
 - C. 0101010

FSM Exercise 1b

 - How many bits do we need to represent all the states in this FSM?
 - Using regular, non-alternative methods
- Write the T.T. for this FSM
- Write the next-state functions for this FSM
- Design the digital logic circuit to implement this FSM, showing all inputs and all outputs




FSM Exercise 2

- Design a FSM that takes in 2 single-bit binary inputs, A and B and always is reset to (begins in) an initial state.
 - The machine will move from the initial state only if **A&&B** is true. Once it does that, however, it will go through N states sequentially, once for every time **A || B** is true.
 - On the last state, it simply goes to the initial state again and repeats.
- A. Draw the state diagram for $N = 3$.
- B. Using the “one-hot method”,** how many bits do we need to represent all the states in this FSM?
- C. Write the next-state functions for this FSM using the approach in B.
- D. Design the dig. logic circuit to implement the FSM using your results so far

FSM Exercise 3

- Consider the FSM circuit, shown here using the “one-hot method”

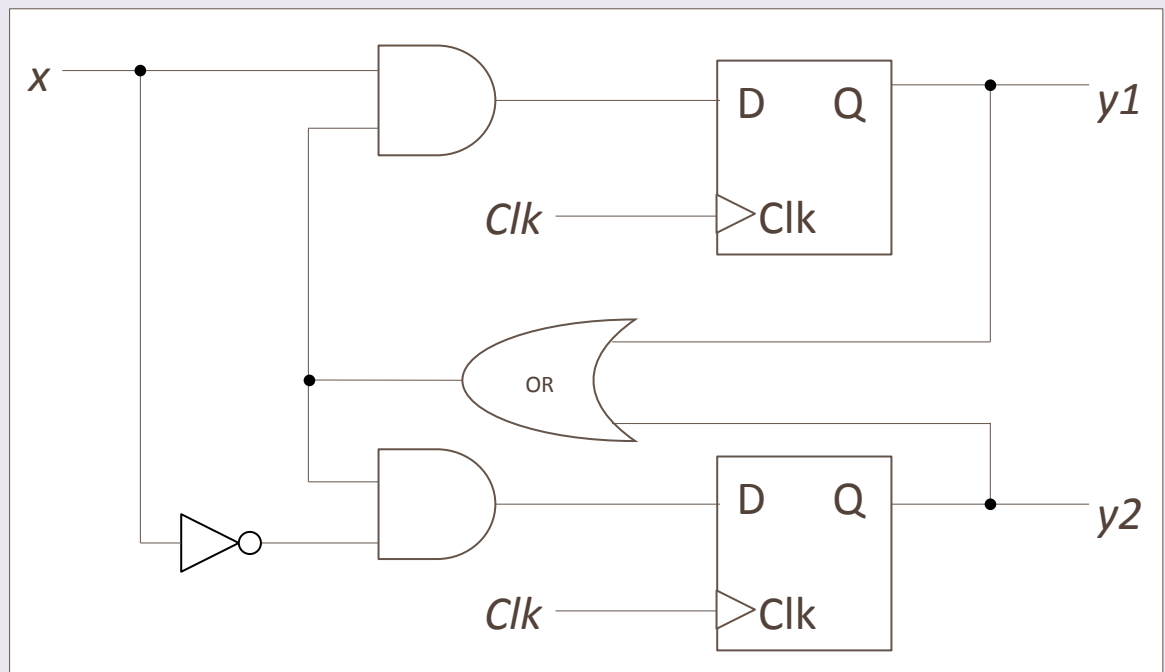- Identify the non-clock inputs and outputs
- Write the next state equations
- Write the T.T. for this FSM
- Draw the state diagram for this FSM



Your To Dos

- Lab #9 due Friday
- Bring your questions re: Final on Thursday

</LECTURE>